

Design of a Band Stop Filter (BSF) using Single stub:

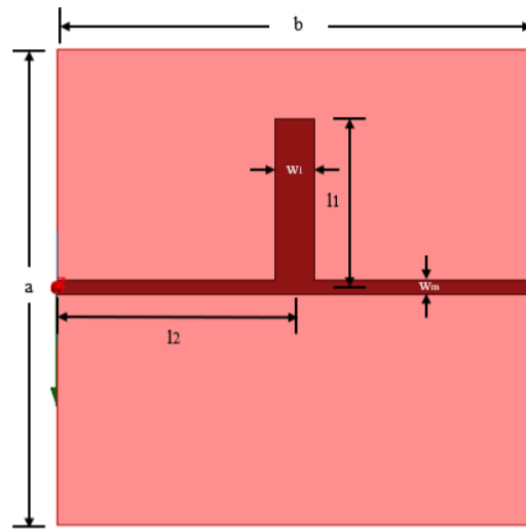


Fig 3. Layout of Single Stub BSF

The layout of the BSF using a Single Open Shunt Stub is shown in fig 3. The problem is to design the BSF using Microstrip line technology using ADS.

➤ Components:

➤ Metal: **Copper**

- Conductivity: 58000000 Siemens/m
- Relative Permittivity (ϵ_r): 1

➤ Substrate: **Rogers RO4003C**

- Relative Permittivity (ϵ_r): 3.55
- Dielectric Loss Tangent ($\tan\delta$): 0.0027

➤ Design Specifications:

- Substrate Thickness = 0.508mm
- Metal Thickness = 0.017mm
- $L1 = 5.494\text{mm}$
- $W1 = 3.016\text{mm}$
- $L2 = 3.197\text{mm}$
- $Wm = 1.136\text{mm}$

➤ **Design Criteria:**

Operating Frequency: 7.8 GHz

➤ **Schematic of BSF:**

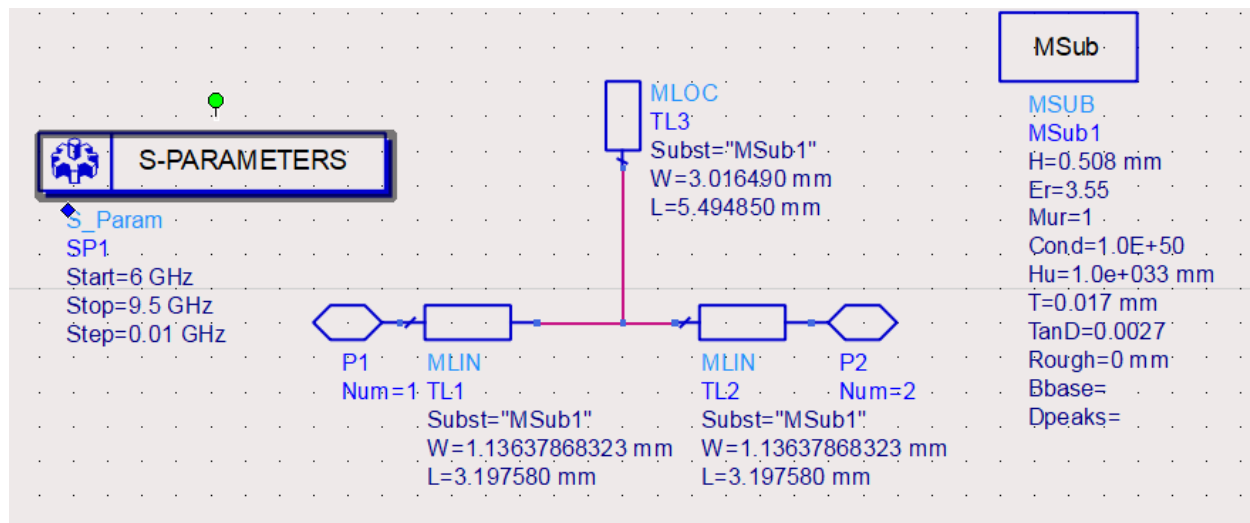


Fig 4. Schematic of Single Stub BSF

➤ **Momentum Layout:**

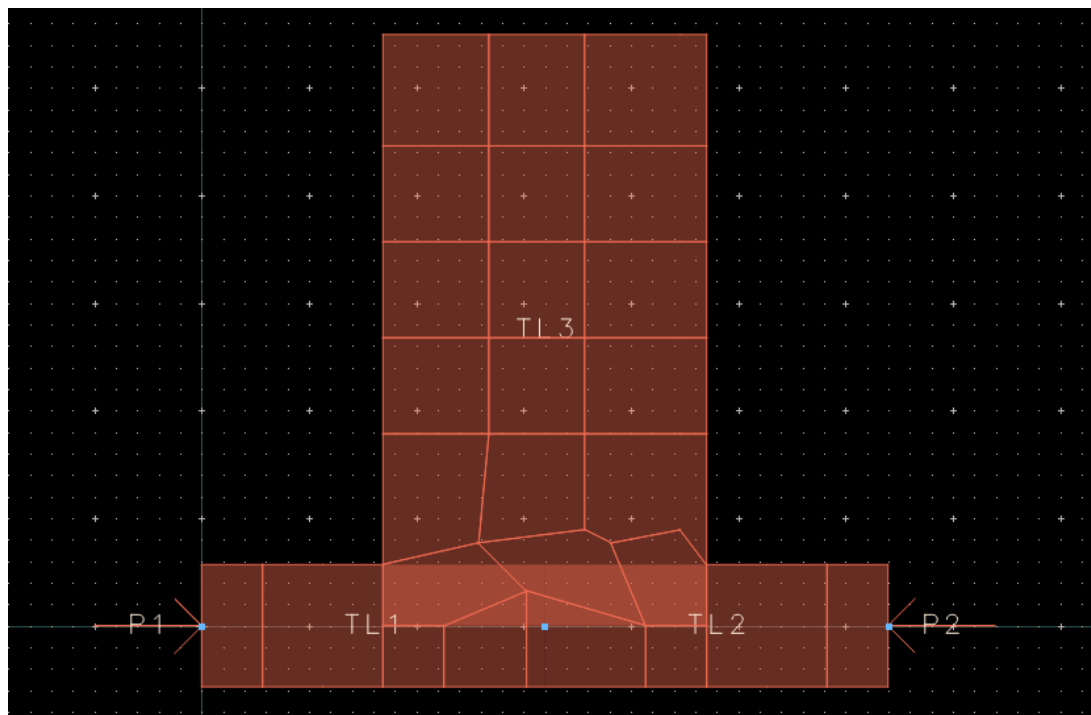


Fig 5. Layout of Single Shunt Open Stub BSF.

➤ **Momentum 3D Layout**

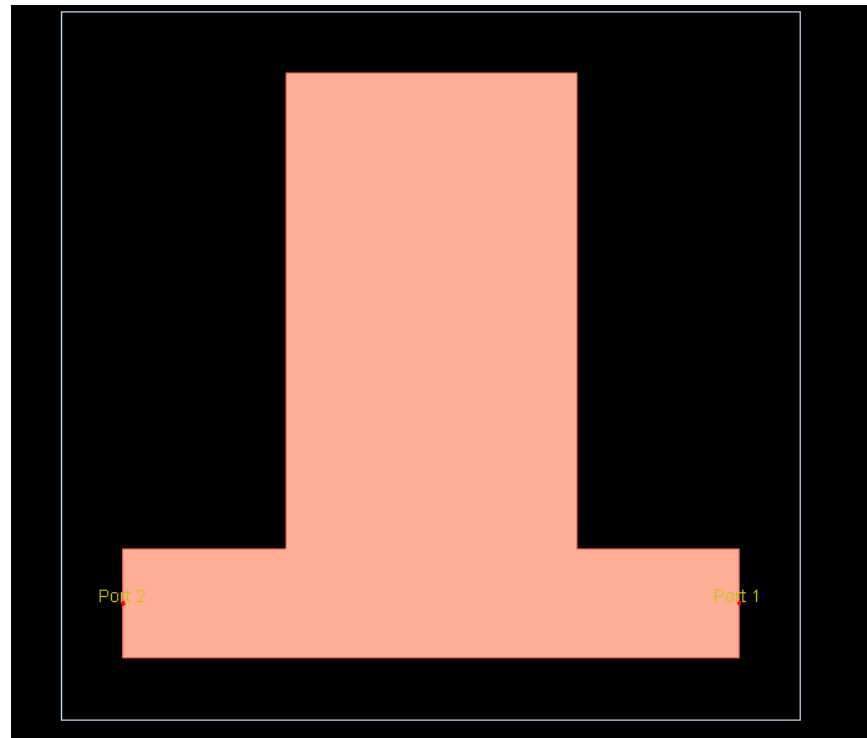


Fig 5. Momentum Layout of BSF

➤ **Substrate Diagram of ADS:**

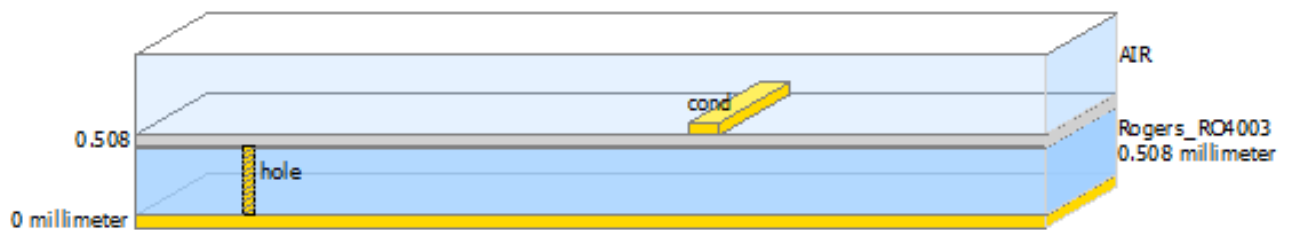


Fig 6. Diagram of the substrate (Dielectric constant 3.55, Rogers_RO4003C, Freq 7.8 GHz)

➤ **Results**

➤ **Magnitude plot of S11 and S21 parameters**

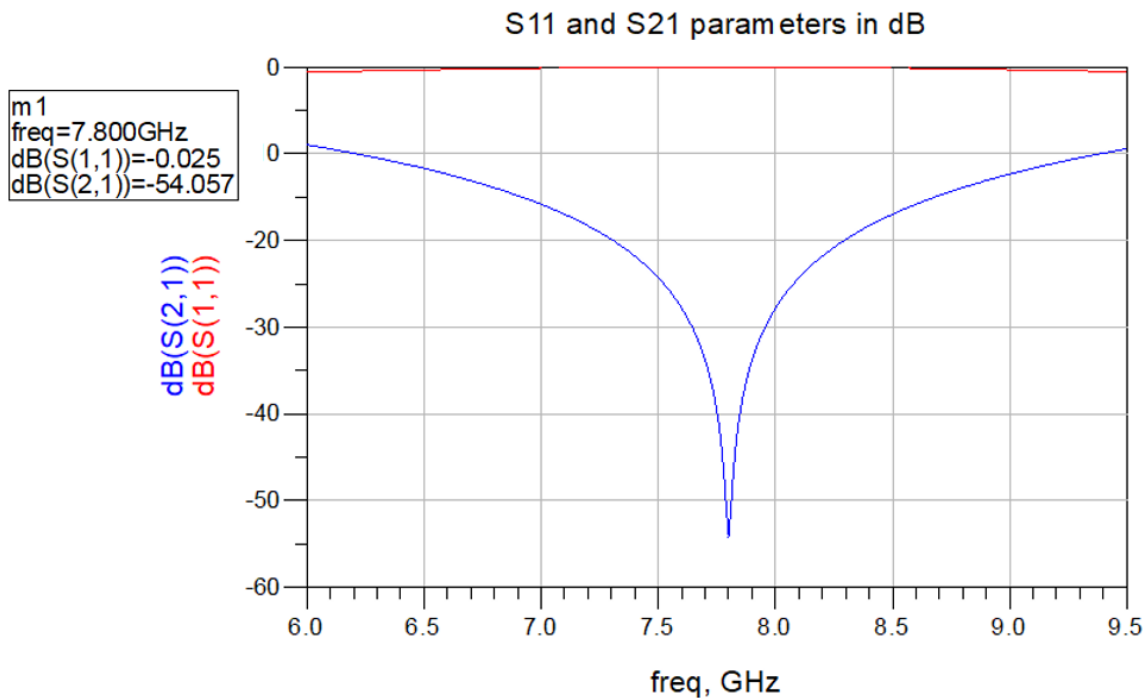


Fig 7. Magnitude plots of S11 and S21 parameters.

➤ **Calculations**

- The characteristics impedance of the shunt open stub line is kept as 25Ω .
- The electric length of the open stub is kept as 90 degree which implies its length is equal to the quarter of the operating wavelength.

➤ **Conclusion:**

- We successfully used ADS to design a BSF using single open stub with microstrip line at the center frequency of 7.8 GHz
- The dip of -54.057 dB for the S21 parameter is a clear indication that the signal is not passed at the respective frequency.
- By using a shunt open stub at electric length of 90 degree we manage to make the input impedance towards the source size to be infinite for the frequency of 7.8 GHz.